



Sharif University of Technology  
Department of Computer Engineering

# Digital System Design

## Gate-level modelling

Siavash Bayat-Sarmadi


# Outline

2


- Gate types
  - ▣ Basic gates
  - ▣ Three-state
  - ▣ Structural design using primitive gates
- Gate delays
  - ▣ Gate-level delay types
  - ▣ Gate-level delay syntax

# Basic Gates


3

 


and

 

nand

 

or

 

nor



xor



xnor



# Instantiation Syntax

4

- Similar to instantiating modules
- Name optional for these primitives
- Example

```
wire OUT, IN1, IN2, IN3;  
and a2input(OUT, IN1, IN2);
```

```
and (OUT, IN1, IN2, IN3);
```

  

# 4-Value Truth Table

5

## □ Example

and	0	1	X	Z	xnor	0	1	X	Z
0	0	0	0	0	0	1	0	X	X
1	0	1	X	X	1	0	1	X	X
X	0	X	X	X	X	X	X	X	X
Z	0	X	X	X	Z	X	X	X	X

# Buf and Not Gates

6

## □ Input

- ▣ Last port in terminal list



## □ Outputs

- ▣ All other ports

## □ Example

- ▣ `buf b1_2out (OUT1, OUT2, IN);`

- ▣ `not (OUT1, IN); //Legal`

  

# 4-Value Truth Table



7

buf	in	out
	0	0
	1	1
	X	X
	Z	X



not	in	out
	0	1
	1	0
	X	X
	Z	X

# Three-state Logic Gates

8

  
  
```
bufif1 b1 (out, in, ctrl);    notif1 n1 (out, in, ctrl);
```



```
bufif0 b1 (out, in, ctrl);    notif0 n1 (out, in, ctrl);
```



# Array of Instances


9

```
wire [2:0] OUT, IN1,  
        IN2;
```

```
nand n0 (OUT[0],  
        IN1[0], IN2[0]);
```

```
nand n1 (OUT[1],  
        IN1[1], IN2[1]);
```
 
```
nand n2 (OUT[2],  
        IN1[2], IN2[2]);
```




```
wire [2:0] OUT,  
        IN1, IN2;
```

```
nand n [2:0] (OUT,  
        IN1, IN2);
```
 
# Example: SR Latch

10

```
module SR_latch(Q,  
Qbar, S,  $\overline{R}$ , En);  
  
output Q, Qbar;  
input S, R, En;  
wire Sbar, Rbar;  
nand n1(Sbar, S, En),  
      n2(Rbar, R, En),  
      n3(Q, Sbar, Qbar),  
      n4(Qbar, Rbar, Q);  
endmodule
```



# Example

11

```
module Top;
  wire q, qbar;
  reg set , reset , en;
  SR_latch l1(q, qbar, set, reset, en);
  initial
  begin
    $monitor($time, "set = %b, reset= %b, en=%b,
    q= %b\n", set, reset, en, q);

    set = 0; reset = 0 ; en = 1;
    #10 reset = 1;
    #10 reset = 0;      #10 set = 1;
    #10 set = 0; reset = 1;
    #10 set = 0; reset = 0 ; en= 0;
    #10 set = 1; reset = 0;
  end
endmodule
```

◆ /Top/q  
◆ /Top/qbar  
◆ /Top/set  
◆ /Top/reset  
◆ /Top/control

St0  
St1  
0  
0  
0



Transcript

File Edit View Bookmarks Window Help



Transcript



```
add wave -position insertpoint sim:/Top/*
```


```
VSIM 3> run
```

```
#           0 set = 0, reset= 0, control=1, q= x
#
#           10 set = 0, reset= 1, control=1, q= 0
#
#           20 set = 0, reset= 0, control=1, q= 0
#
#           30 set = 1, reset= 0, control=1, q= 1
#
#           40 set = 0, reset= 1, control=1, q= 0
#
#           50 set = 0, reset= 0, control=0, q= 0
#
#           60 set = 1, reset= 0, control=0, q= 0
#
run
```

# Example: Multiplexer

13

## □ 4-to-1 Multiplexer

 

# Example (cont'd.)

14

```
module mux4_to_1 (output out, input i0, i1, i2, i3, s1, s0);  
    wire s1n, s0n;  
    wire y0, y1, y2, y3;  
    not (s1n, s1);  
    not (s0n, s0);  
    and (y0, i0, s1n, s0n);  
    and (y1, i1, s1n, s0);  
    and (y2, i2, s1, s0n);  
    and (y3, i3, s1, s0);  
    or (out, y0, y1, y2, y3);  
endmodule
```

# Example (cont'd.)

15

```
module stimulus;
reg i0, i1, i2, i3, s1, s0;
wire out;
mux4_to_1 my_mux(out,i0,i1,i2,i3,s1,s0);
initial begin i0 = 0;i1 = 1;i2 = 0; i3 = 1;
#1 $display("i0=%b, i1=%b, i2=%b, i3=%b\n",
,i0,i1,i2,i3);
s1 = 0; s0 = 0;
#1 $display("s1=%b, s0=%b, out=%b\n",
s1,s0,out);
```

# Example


16

```
s1 = 0; s0 = 1;
#1 $display("s1=%b, s0=%b, out=%b\n"
,s1,s0,out);
s1 = 1; s0 = 0;
#1 $display("s1=%b, s0=%b, out=%b\n"
,s1,s0,out);
s1 = 1; s0 = 1;
#1 $display("s1=%b, s0=%b, out=%b\n"
,s1,s0,out);
end
endmodule
```



# Example

17

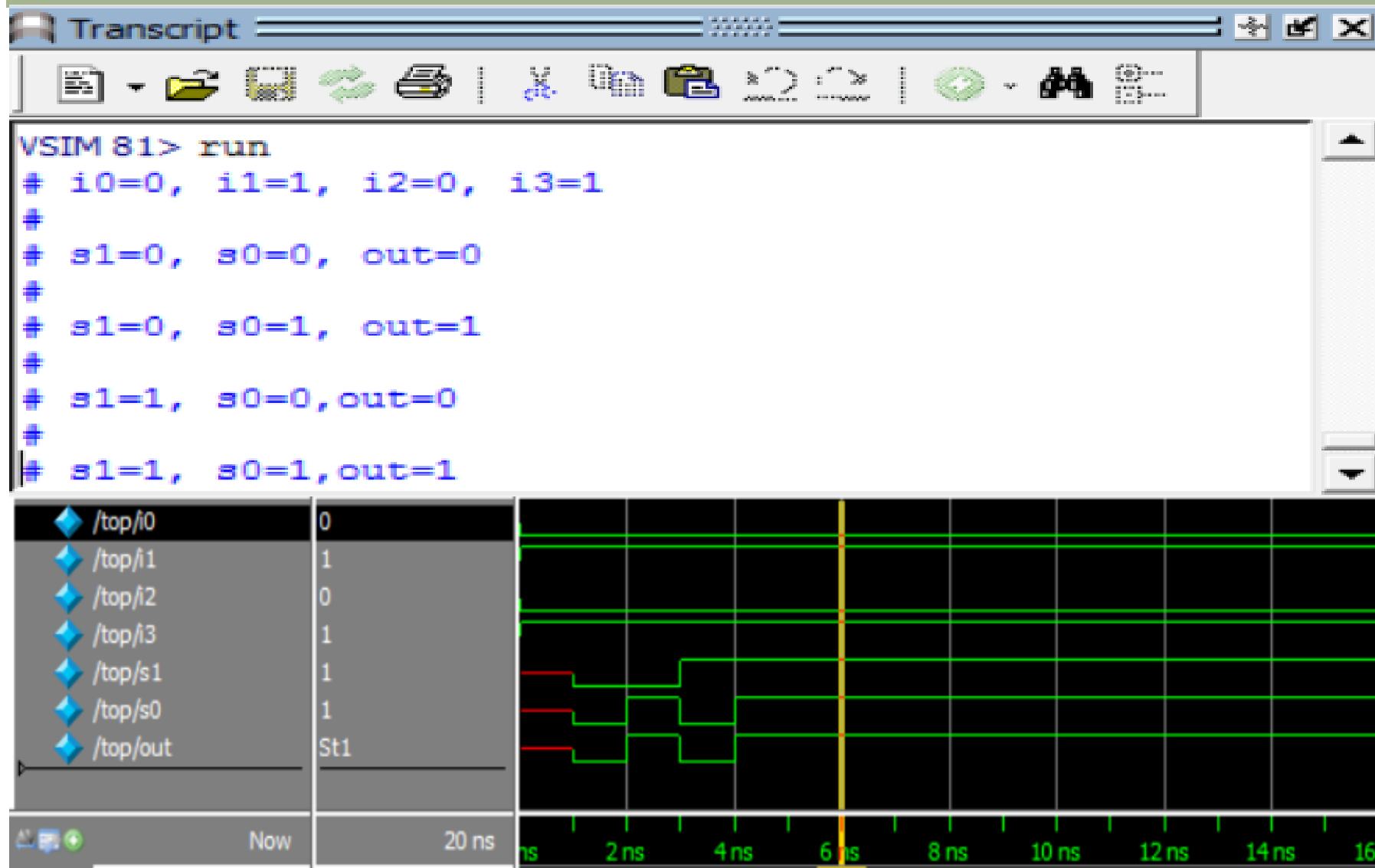

# Gate Delays


18

- Types of delay
- Gate-level delay
- Gate-level syntax


# Types of delay

19

## □ Rise delay

 

## □ Fall delay

 

# Types of delay (cont'd.)

20

- Turn-off delay
  - ▣ Gate output transition to **z** from other values
- If one delay specified
  - ▣ Same delay for all transitions
- If two
  - ▣ Assigned to rise and fall
  - ▣ turn-off = min (rise, fall)
- Minimum of the three is considered for a transition to **x**

# Example

21

- One delay specified
  - ▣ and `#(delay_time) a1(out, i1, i2);`
- Two delays specified
  - ▣ and `#(rise_val, fall_val) a2(out, i1, i2);`
- Three delays specified
  - ▣ `bufif0 #(rise_val, fall_val, turnoff_val) b1`  
`(out, in, control);`

# Min, Typ and Max Values

22

- Each delay type can have 3 values
  - ▣ Minimum
  - ▣ Typical
  - ▣ Maximum
- Only one value used during a simulation
  - ▣ Chosen at the start
  - ▣ Typical used if not specified

# Example

23

```
/*  
one delay,  
if mindelays chosen -> delay = 4  
if typdelays chosen -> delay = 5  
if maxdelays chosen -> delay = 6  
*/  
bufif1 # (4:5:6) b1 (t1, in1, ctrl1);
```

# Example

24

```
/*  
two delays  
if mindelays chosen -> rise=4,fall=3,turn-  
off=3  
if typdelays chosen -> rise=5,fall=4,turn-  
off=4  
if maxdelays chosen -> rise=6,fall=5,turn-  
off=5  
*/  
bufif1 # ( 4:5:6,3:4:5) b2(t2,in2,ctrl2);
```



# Example

25

```
/*  
three delays  
  if mindelays chosen -> rise=1,fall=2,turn-  
off=1  
  if typdelays chosen -> rise=2,fall=3,turn-  
off=2  
  if maxdelays chosen -> rise=3,fall=4,turn-  
off=3  
*/  
bufif1 # (1:2:3, 2:3:4, 3:4:5 ) b3  
(t3, In3, ctrl3);
```

# Example

26

The screenshot displays the ModelSim interface. The top toolbar contains various icons for file operations, simulation control, and viewing. Below the toolbar, the 'Transcript' window shows the command sequence: `ModelSim> vsim -novopt work.buif +typdelay`, `# vsim +typdelay -novopt work.buif`, `# Loading work.buif`, and `add wave -position insertpoint sim:/buif/*`. The main editor window shows the Verilog code for a module named `buif`. The code includes a `wire out`, registers `in` and `ctrl`, and a `bufif1` component. The initial values are set to 1 for both `in` and `ctrl`. The bottom window shows a timing diagram with a vertical yellow cursor at 2 ns. The signal list on the left includes `/buif/out`, `/buif/in`, and `/buif/ctrl`. The timing diagram shows a red signal for `out` and green signals for `in` and `ctrl`. The time scale is marked from 0 ns to 14 ns in 2 ns increments.

```
ModelSim> vsim -novopt work.buif +typdelay
# vsim +typdelay -novopt work.buif
# Loading work.buif
add wave -position insertpoint sim:/buif/*
```

```
Ln#
1 module buif;
2   wire out;
3   reg in,ctrl;
4   bufif1 #(1:2:3, 2:3:4, 3:4:5 ) b (out,in,ctrl);
5   initial begin
6     in = 1 ; ctrl = 1;
7   end
8   endmodule
-
```

Signal	Value
/buif/out	St1
/buif/in	1
/buif/ctrl	1


Now 20 ns  
Cursor 1 2 ns

2 ns 4 ns 6 ns 8 ns 10 ns 12 ns 14 ns
 
# Delay example

27

```
module D (out, a, b, c);  
  output out;  
  input a, b, c;  
  
  wire e;  
  
  and # (5)  a1 (e, a, b);  
  or  # (4)  o1 (out, e, c);  
  
endmodule
```



# Delay example (cont'd.)



28

```
module stimulus;
reg A,B,C;
wire OUT;
D d1 (OUT,A,B,C);
initial begin
    A = 1'b0; B=1'b0; C = 1'b0;
    #10 A = 1'b1; B = 1'b1; C = 1'b1;
    #10 A = 1'b1; B = 1'b0; C = 1'b0;
    #20 $finish;
end
endmodule
```

# Delay example (cont'd.)

29

## □ Delay simulation waveform

 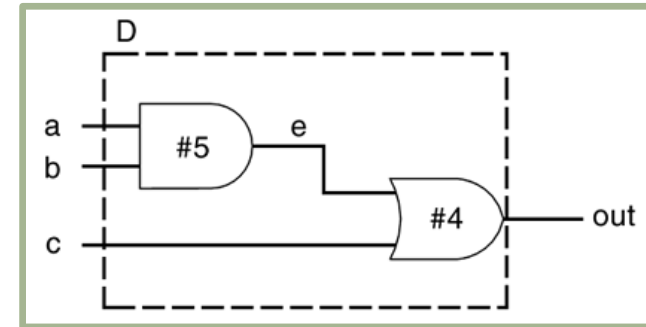

# Generate Blocks

30

- Dynamic generation
  - ▣ At elaboration time
  - ▣ Before the simulation begins
- Keywords
  - ▣ generate
  - ▣ endgenerate

# Generate Blocks (Cont'd.)

31

- What can be instantiated
  - ▣ **Variable declarations**
  - ▣ **Modules**
  - ▣ **Gate primitives**
  - ▣ ...

# Generate Blocks (Cont'd.)

32

- Allowed in the generate scope
  - ▣ Variable declaration
  - ▣ Parameter redefinition
  - ▣ ...
- Not permitted in a generate statement
  - ▣ parameters, local parameters declarations
  - ▣ input, output, inout declarations
  - ▣ ...



# Generate Blocks (Cont'd.)

33

- Particularly convenient when
  - ▣ The same operation or module instance is repeated
    - generate loop
  - ▣ Certain code is conditionally included based on parameter definitions
    - generate conditional
    - generate case

# Generate loop

34

```
genvar i;  
generate  
    for  
    begin  
        //statement  
    end  
endgenerate
```

- **genvar** can be defined only in a generate loop
- Generate loops can be nested

# Example 1

35

```
module bitwise_xor (out, i0, i1);  
parameter N = 32;  
output [N-1:0] out;  
input [N-1:0] i0, i1;  
genvar j;  
generate for (j=0;j<N;j=j+1) begin:xor_loop  
    xor g1 (out[j], i0[j], i1[j]);  
end  
endgenerate  
endmodule
```

## Example 2 (Cont'd.)

36

```
module ripple_adder(co, sum, a0, a1, ci);  
parameter N = 4; //4-bit bus by default  
//port declarations  
output [N-1:0] sum;  
output co;  
input [N-1:0] a0 ,a1;  
input ci;  
wire [N-1:0] carry; //Local wire declaration  
//Assign 0th bit of carry equal to carry  
//input  
buf b1 (carry[0], ci);
```

## Example 2 (Cont'd.)

37

```
genvar i;
generate for (i=0; i<N; i=i+1) begin:r_loop
    wire t1, t2, t3;
    xor g1 (t1, a0[i], a1[i]);
    xor g2 (sum[i], t1, carry[i]);
    and g3 (t2, a0[i], a1[i]);
    and g4 (t3, t1, carry[i]);
    or  g5 (carry[i+1], t2, t3);
end//end of the for loop
endgenerate//end of the generate block
buf b2 (co, carry[N]);
endmodule
```

# Example 2 (Cont'd.)

38

- genvar i
  - ▣ A temporary loop variable
  - ▣ Used only in the evaluation of the generate block
  - ▣ Does not exist during the simulation
    - generate loops are unrolled before simulation

# Example 2 Hierarchical instance names

39

Xor	And	Or
<code>r_loop[0].g1</code>	<code>r_loop[0].g3</code>	<code>r_loop[0].g5</code>
<code>r_loop[1].g1</code>	<code>r_loop[1].g3</code>	<code>r_loop[1].g5</code>
<code>r_loop[2].g1</code>	<code>r_loop[2].g3</code>	<code>r_loop[2].g5</code>
<code>r_loop[3].g1</code>	<code>r_loop[3].g3</code>	<code>r_loop[3].g5</code>
<code>r_loop[0].g2</code>	<code>r_loop[0].g4</code>	
<code>r_loop[1].g2</code>	<code>r_loop[1].g4</code>	
<code>r_loop[2].g2</code>	<code>r_loop[2].g4</code>	
<code>r_loop[3].g2</code>	<code>r_loop[3].g4</code>	

# Example 2 Hierarchical instance names (Cont'd.)

40

- Generated instances are connected with the following generated nets

<code>r_loop[0].t1</code>	<code>r_loop[0].t2</code>	<code>r_loop[0].t3</code>
<code>r_loop[1].t1</code>	<code>r_loop[1].t2</code>	<code>r_loop[1].t3</code>
<code>r_loop[2].t1</code>	<code>r_loop[2].t2</code>	<code>r_loop[2].t3</code>
<code>r_loop[3].t1</code>	<code>r_loop[3].t2</code>	<code>r_loop[3].t3</code>



# Generate Conditional

41

```
module multiplier (product, a0, a1);  
parameter a0_width = 8;  
parameter a1_width = 8;  
localparam product_width =  
a0_width + a1_width;  
  
output [product_width-1:0] product;  
input [a0_width-1:0] a0;  
input [a1_width-1:0] a1;
```

# Generate Conditional

42

**generate**

```
if ((a0_width < 8) || (a1_width < 8))  
    cla_multiplier #(a0_width,a1_width)  
    m0 (product, a0, a1);
```

**else**

```
    tree_multiplier #(a0_width,a1_width)  
    m0 (product, a0, a1);
```

**endgenerate**

**endmodule**